

CIRCUITS DAY 1: ELECTRIC CURRENT & CHARGE FLOW


CED 11.1 · Skill 3.B · FRQ: QQT

PREDICT BEFORE OBSERVING

Ammeter A_1 is just before a bulb and A_2 is just after it in the same loop. Circle one: **A_2 is smaller / A_2 is equal / A_2 is larger / A_2 is zero.** Be ready to defend your choice.

Observation source: battery–bulb loop with a movable ammeter; projected PhET *Circuit Construction Kit: DC* as an exact substitute for this observation; or the printed circuit below.

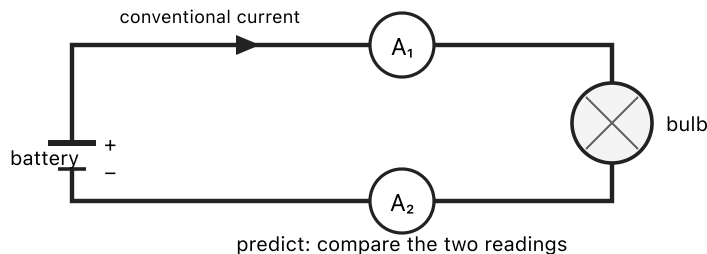PRINTED FALLBACK — PREDICT THE TWO READINGS




CURRENT IS A RATE

Electric current is the rate at which charge crosses a chosen cross section.

$$I = \frac{\Delta Q}{\Delta t} \quad 1 \text{ A} = 1 \text{ C/s}$$

QUICK A total charge of 18 C crosses a point in 12 s. Find the average current and carry the units through the division.

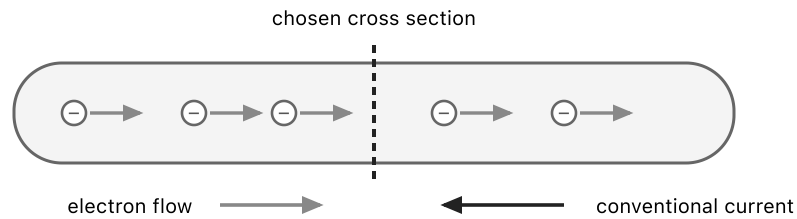CURRENT DIRECTION AND ELECTRON FLOW**DIRECTION OF CURRENT VS. DIRECTION OF ELECTRON FLOW**

The arrows on the electrons show electron flow to the right. Conventional current is defined in the opposite direction, to the left.

- Current is not a vector, but a circuit current has a direction around the path.
- Conventional current is defined as the direction positive charge would move.
- In metal wires, electrons flow opposite the conventional-current direction.
- With zero current, electrons still have microscopic thermal motion; their net electron flow is zero.

WE DO A wire carries 0.80 A. Find the magnitude of charge crossing a point in 25 s.


YOU DO For that same current, how many electrons cross per second? Use $e = 1.60 \times 10^{-19} \text{ C}$.

CHARGE IS CONSERVED AROUND ONE LOOP

In a steady series circuit, charge does not accumulate in any element. Therefore the current is the same at every point in the loop.

$$I_{\text{before}} = I_{\text{through}} = I_{\text{after}}$$

The bulb receives electrical energy and transfers it to light and thermal energy. The moving charges continue through the circuit.

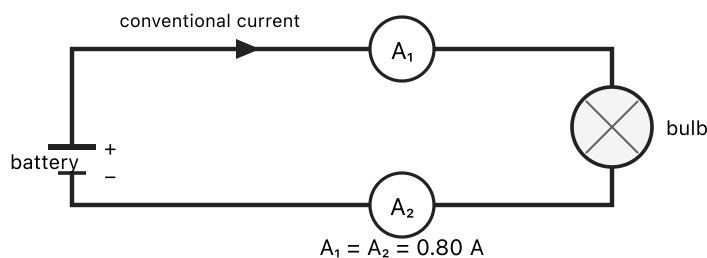USE ONE CURRENT LABEL AROUND THE LOOP

REASON A student claims that a 0.80 A current before the bulb becomes 0.50 A afterward. Calculate the charge that would accumulate in the bulb in 20 s if that claim were true.

Signal and drift: charge carriers are already present throughout the wire. Closing the switch establishes an electric field through the connected circuit; it does not require one electron to race from the battery to the bulb.

PRACTICE

1. A current of 0.65 A flows for 40 s . Find the charge that crosses one point.

2. A pulse transfers 7.2 C in 4.0 s . Find the average current.

3. A 0.60 A current is carried by electrons. Find the number of electrons crossing a section each second.

4. An ammeter before a bulb reads 1.25 A . What should an ammeter after the bulb read in the same steady series loop? Explain.

5. Draw arrows for conventional current and electron flow on a battery–wire–bulb loop. State why the arrows point in opposite directions.

