

CIRCUITS DAY 14: RC CIRCUITS: INITIAL STATE, STEADY STATE & TIME CONSTANT


CED 11.8 · Skill 1.C · FRQ: TBR

PREDICT THE PHENOMENON

A bulb is in series with a resistor and an initially uncharged capacitor. The switch closes. Is the current largest **immediately / long after / the same at all times**?

Observation source: a safe charging demonstration, the site RC bench, or the paired state sketches.

SAME BRANCH AT TWO LIMITING TIMES

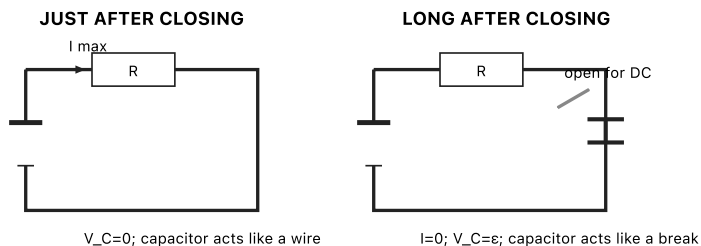

Always name the time before simplifying an RC circuit.

NOTES / REASONING

INITIAL AND STEADY-STATE MODELS

At $t=0^+$: an initially uncharged capacitor has $V_C = 0$, so it acts like a wire and current is maximum.


At steady state: $V_C = \varepsilon$, so the capacitor branch carries no DC current and acts like a break.

WE DO For $\varepsilon = 10 \text{ V}$ and $R = 25 \text{ k}\Omega$, find initial and steady-state current.

THE TIME CONSTANT

$$\tau = RC$$

At one time constant, a charging capacitor reaches about 63% of its final voltage. A discharging capacitor has about 37% of its initial voltage remaining.

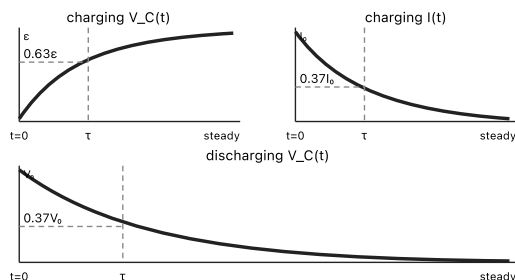QUALITATIVE RC TRACES

CALCULATE For $R = 25 \text{ k}\Omega$ and $C = 200 \text{ }\mu\text{F}$, find τ , $V_C(\tau)$, and the charging current at τ . Use the 63%/37% landmarks.

PRACTICE

1. A $15\text{ k}\Omega$ resistor and $400\text{ }\mu\text{F}$ capacitor form an RC branch. Find τ .

2. A 12 V capacitor discharges. Estimate its voltage after one τ .

3. For a 9 V source and $30\text{ k}\Omega$ resistor, find the initial charging current.

4. Sketch $V_C(t)$ and $I(t)$, label $t=0$, one τ , and steady state.