

ELECTRICITY DAY 14: CAPACITORS - CAPACITANCE, ENERGY & DIELECTRICS

CED 10.6–10.7 · Skill 2.B · FRQ: MR · target: capacitance is set by geometry and material, not by applied voltage

PREDICT BEFORE OBSERVING

A charged capacitor is disconnected from its source and connected across a small bulb. Predict: **steady light / brief flash / no light**. State where the delivered energy was stored.

Observation source: a low-voltage capacitor and bulb/LED with appropriate resistor; projected circuit simulation; or the printed sequence: charged capacitor → connect bulb → flash → uncharged capacitor.


CAPACITANCE

$$C = Q/\Delta V \quad Q = C\Delta V$$

For an ideal linear capacitor, C is a device property. Changing the applied voltage changes Q in the same ratio, so $Q/\Delta V$ remains constant.

QUICK A $0.40 \mu\text{F}$ capacitor is connected first to 10 V and then to 20 V. Compare Q and C in the two cases.

PARALLEL-PLATE CAPACITOR MODEL

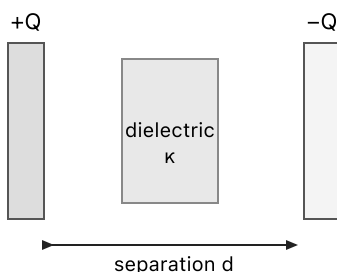

$$C = \epsilon_0 \kappa A/d$$

larger $A \rightarrow$ larger C

larger $d \rightarrow$ smaller C

larger $\kappa \rightarrow$ larger C

PARALLEL-PLATE GEOMETRY

$$C = \epsilon_0 \kappa A / d \quad \epsilon_0 = 8.85 \times 10^{-12} \text{ F/m}$$

Use plate overlap area A in m^2 and separation d in m . For vacuum/air, $\kappa \approx 1$.

WE DO A capacitor has plate area 150 cm^2 , separation 1.5 mm , and dielectric constant $\kappa = 2.5$. Find C in pF .

YOU DO For the same capacitor, find Q when connected to 90 V .

Geometry prediction: doubling A doubles C ; doubling d halves C ; inserting a dielectric multiplies C by κ .

STORED ENERGY

$$U_C = \frac{1}{2}Q\Delta V = \frac{1}{2}C(\Delta V)^2 = \frac{Q^2}{2C}$$

WE DO Find the stored energy of the 221 pF capacitor at 90 V. Report J and μJ .

ENERGY THROUGH A POTENTIAL DIFFERENCE

For a charge moving through a potential difference:

$$\Delta U = q\Delta V \quad W_{\text{field}} = -\Delta U$$

YOU DO A $+2.0\mu\text{C}$ charge moves from 150 V to 0 V through a circuit element. Find ΔU and the energy delivered by the electric field.

REPRESENT Draw before/after energy bars for the capacitor-bulb flash. Include stored electric energy, light/thermal transfer, and final capacitor energy.



PRACTICE

1. A capacitor stores $6.0 \mu\text{C}$ at 24 V . Find C .

2. Vacuum plates have $A = 180 \text{ cm}^2$ and $d = 2.0 \text{ mm}$. Find C in pF .

3. A $120 \mu\text{F}$ capacitor is charged to 15 V . Find stored energy in mJ .

4. Plate area doubles, separation triples, and κ becomes four times larger. Find the C factor.

5. A dielectric is inserted. Compare Q , V , C , and U for (a) a capacitor still connected to an ideal battery and (b) an isolated charged capacitor. State what is conserved in each case.