

CIRCUITS DAY 5: RC CIRCUITS

WARMUP The Feedback Loop

A charged capacitor discharges through a resistor. The charge drives the current, and the current drains the charge. Predict the shape of $q(t)$: **steady fall to zero** / **fast at first, then ever slower** / **slow at first, then speeding up**? Circle one, and use that feedback to say why.

RC CIRCUITS: THE EXPONENTIAL UNIT

Discharge: loop rule $q/C = IR$ with $I = -dq/dt$ gives $dq/dt = -q/RC$, so

$$q(t) = Q_0 e^{(-t/\tau)}, \quad \tau = RC \text{ (seconds — check: } \Omega \cdot F = s)$$

Charging toward a battery $\mathcal{E}$: $q(t) = C\mathcal{E}(1 - e^{(-t/\tau)})$ — same τ , approaching full instead of empty.

Landmarks: at $t = \tau$, 63% of the change is done; at 5τ , 99.3%. I , V , and q all share the same exponential clock.

WE DO Exercise 1: The Clock

$C = 2.0 \mu\text{F}$ charged to 12 V discharges through $R = 1.0 \text{ M}\Omega$. **(a)** $\tau = RC =$ _____ s. **(b)** $I_0 = V_0/R =$ _____ μA . **(c)** Total charge released $= CV_0 = I_0\tau =$ _____ μC (both products!).

READING THE EXPONENTIAL

WE DO Exercise 2: Evaluate the Curve

For Exercise 1's discharge ($Q_0 = 24 \mu\text{C}$, $\tau = 2.0 \text{ s}$): **(a)** q at $t = 2.0 \text{ s}$: _____ μC . **(b)** q at $t = 4.0 \text{ s}$: _____ μC . **(c)** When is $q = 12 \mu\text{C}$? $t = \tau \ln 2 =$ _____ s.

YOU DO Exercise 3: Charging Up

The same RC pair ($\tau = 2.0 \text{ s}$) now CHARGES from a 12 V battery: $q(t) = 24(1 - e^{-(t/2)}) \mu\text{C}$. Find q at $t = 2.0 \text{ s}$, and the current at $t = 0$ (the capacitor starts as a bare wire!).

CALC Exercise 4: Derive the Discharge

Start from the loop rule $q/C - IR = 0$ with $I = -dq/dt$. Separate variables ($dq/q = -dt/RC$), integrate both sides, and exponentiate to reach $q(t) = Q_0 e^{-(t/RC)}$. Show where the initial condition enters.

PAPER PRACTICE

PRACTICE PROBLEMS

P1 The Time Constant

$R = 500 \text{ k}\Omega$, $C = 4.0 \text{ }\mu\text{F}$. Find τ .

P2 Initial Current

A $3.0 \text{ }\mu\text{F}$ capacitor at 9.0 V discharges through $1.5 \text{ M}\Omega$. Find I_0 in μA .

P3 One Tau Later

For P2's circuit, how much charge remains on the capacitor at $t = \tau$? ($q = Q_0 e^{-1}$.)

P4 Where the Energy Went

P2's capacitor stored $U = \frac{1}{2}CV^2$ initially. Compute U — and state where ALL of it is by $t \gg \tau$. (Day 2's integral $\int I^2 R \, dt$ collects exactly this much heat; no derivation needed, just the argument.)