

CIRCUITS DAY 7: UNIT REVIEW

BIG IDEAS TO REMEMBER

- $I = dq/dt$, $Q = \int I dt$; $R = \rho L/A$; $V = IR$.
- $P = IV = I^2 R = V^2/R$; $E = \int P dt$; the kWh is 3.6×10^6 J.
- **Series adds R** (same I); **parallel adds $1/R$** (same V) — capacitors flipped.
- **Kirchhoff**: junctions conserve charge; loops close because potential is single-valued. Real battery: $I = \varepsilon/(R+r)$, $V_{\text{term}} = \varepsilon - Ir$.
- **RC**: $\tau = RC$; discharge $Q_0 e^{-(t/\tau)}$, charge $C\varepsilon(1 - e^{-(t/\tau)})$; 63% at τ , 99.3% at 5τ .

A Rules Rapid-Fire

One-line answers: **(a)** Two identical resistors: series R_{eq} vs parallel R_{eq} — ratio? **(b)** Why does the SMALLER parallel branch carry MORE current? **(c)** At $t = 0$, a charging capacitor acts like what circuit element? At $t \gg \tau$? **(d)** What does a voltmeter read across an ideal battery delivering current — and a real one?

MIXED PRACTICE

B Network Chain

A 24 V battery drives a $6.0\ \Omega$ resistor in series with $(3.0\ \Omega \parallel 6.0\ \Omega)$. Find R_{eq} , the battery current, the voltage across the parallel pair, the current in each branch, and the power in the series resistor.

C Real-Battery Chain

$\mathcal{E} = 12\text{ V}$, $r = 0.5\ \Omega$, load $R = 5.5\ \Omega$. Find I , V_{term} , the power to the load, the power wasted in the battery, and the efficiency $R/(R+r)$.

D RC Chain

$C = 2.0\ \mu\text{F}$ at 12 V discharges through $R = 1.0\ \text{M}\Omega$. Find τ , I_0 , the charge remaining at $t = 2.0\text{ s}$, and the time for the charge to halve.

E Short FRQ: Derive the Discharge

A capacitor C charged to Q_0 discharges through R .

- a. **Write** the loop rule and convert it to a differential equation in $q(t)$.

- b. **Solve** it by separation of variables, applying the initial condition.

- c. **Show** that the total energy dissipated in R equals the capacitor's initial $\frac{1}{2}Q_0^2/C$ (energy argument, no integral required).

F Reflection

Which of these can you least reliably do on your own — network collapse, Kirchhoff bookkeeping, real batteries, or RC exponentials? Name it, and write your plan to fix it before the test:

Test Reminder: resistor rules are the capacitor rules FLIPPED; the loop rule needs consistent signs (pick a direction and commit); $\tau = RC$ comes out in seconds when R is in Ω and C in F — or in seconds when $M\Omega$ meets μF .