

INDUCTION DAY 5: INDUCTANCE & LR CIRCUITS

WARMUP A Coil Fights Its Own Current

A coil's current makes flux through the coil ITSELF — so changing the current changes its own flux, inducing an EMF in itself that (Lenz!) opposes the change. What everyday mechanics concept does "opposes changes to its own motion-quantity" sound like?

INDUCTANCE: CURRENT INERTIA

$$\mathcal{E}_L = -L \cdot dI/dt \quad (L \text{ in henries; solenoid: } L = \mu_0 n^2 \cdot (\text{volume}))$$

LR decay (switch the battery out): $I(t) = I_0 e^{-(t/\tau)}$ with $\tau = L/R$. **LR rise**: $I(t) = (\mathcal{E}/R)(1 - e^{-(t/\tau)})$ — the inductor starts as an OPEN switch, ends as a bare wire (the capacitor's exact opposite).

Stored energy: $U = \frac{1}{2}LI^2$ — in the magnetic field, the twin of $\frac{1}{2}CV^2$.

WE DO Exercise 1: Clock, Bank, and Flow

$L = 5.0 \text{ H}$ carrying 2.0 A discharges through $R = 10 \Omega$. **(a)** $\tau = L/R =$ _____. **(b)** Stored energy $\frac{1}{2}LI^2 =$ _____. **(c)** Total charge that flows: $I_0 \tau =$ _____.

SELF-EMF AND THE RISE

WE DO Exercise 2: Back-EMF

A 0.2 H inductor's current is ramped at $di/dt = 50 \text{ A/s}$. **(a)** $\epsilon_L = L \cdot di/dt = \underline{\hspace{2cm}}$. **(b)** The ramp doubles to 100 A/s: $\epsilon_L = \underline{\hspace{2cm}}$. **(c)** The current is large but CONSTANT: $\epsilon_L = \underline{\hspace{2cm}}$.

YOU DO Exercise 3: The Rise

A 12 V battery, $R = 10 \, \Omega$, $L = 5.0 \text{ H}$ ($\tau = 0.5 \text{ s}$). Find the FINAL current ($t \gg \tau$, inductor = bare wire), the current at $t = 0$ (inductor = open switch), and the current at $t = \tau$ (63% of the way).

CALC Exercise 4: Derive the Decay

After the switch: the loop rule reads $-L \cdot di/dt - IR = 0$. Separate variables and integrate to reach $I(t) = I_0 e^{(-Rt/L)}$. Compare line-by-line with the RC derivation — same mathematics, new letters.

PAPER PRACTICE

PRACTICE PROBLEMS

P1 The Clock

$L = 2.0 \text{ H}$, $R = 8.0 \Omega$: find τ .

P2 Back-EMF

A 0.5 H inductor with current ramping at 20 A/s : find $|\epsilon_{\text{LI}}|$.

P3 Stored Energy

A 2.0 H inductor carries 3.0 A . Find $U = \frac{1}{2}LI^2$.

P4 Why Switches Spark

Opening a switch on an inductive circuit forces di/dt to be huge (current to zero, fast). Use $\epsilon = -L \cdot di/dt$ to explain the spark that jumps the gap — and why the ENERGY for the spark was already sitting in the circuit before the switch moved.